 




Federal University of Santa Catarina
Department of Electrical Engineering
Integrated Circuits Laboratory



On the minimum supply voltage for CMOS analog circuits: rectifiers and oscillators



Carlos Galup-Montoro, Marcio C. Schneider and Marcio B. Machado



Rectifier outline

- ⇒ Background: microwave power detection
- ⇒ Power/peak detector
- ⇒ Half-wave rectifier
- ⇒ MOSFETs as diodes
- ⇒ Weak inversion MOSFET model

Background: microwave power detection

  


- Basic detector circuit


Wetenkamp, IEEE MTT-S Int.
Microwave Symp. Dig., 1983

Power/Peak Detector 1

A simple case: square-wave input

 

Waveforms for $V_P \gg n\phi_t$

 

Steady-state analysis

Basic principle: charge conservation

$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = 0 \quad I_D = I_0 [e^{\frac{V_D}{n\phi_t}} - 1]$$


$$\frac{I_0}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_p - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_p - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = 0$$

Assumption: very low ripple $\rightarrow V_o \approx$ constant

$$\frac{V_o}{n\phi_t} = \ln \left[\cosh \left(\frac{V_p}{n\phi_t} \right) \right]$$

Power/Peak Detector 2

A simple case: square-wave input

 

$$\frac{V_o}{n\phi_t} = \ln \left[\cosh \left(\frac{V_P}{n\phi_t} \right) \right]$$

Power Detector

$$V_P \ll n\phi_t \rightarrow \frac{V_o}{n\phi_t} \cong \frac{1}{2} \left(\frac{V_P}{n\phi_t} \right)^2$$


Peak Detector

$$V_P \gg n\phi_t \rightarrow V_o \cong V_P - n\phi_t \ln 2$$

Diode "ON" voltage drop
Input

Results for sine input are similar.
Difference is a "form factor"

Half-wave rectifier circuit 1

 

Steady-state analysis (similar to peak detector)


Basic principle: charge conservation

$$\frac{I_0}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_p - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_p - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = I_L$$

Assumption: very low ripple $\rightarrow V_o \approx \text{constant}$

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{\cosh(V_p / n\phi_t)}{1 + I_L / I_0} \right]$$

Half-wave rectifier circuit 2


 


Input



$$V_P > n\phi_t \rightarrow V_o \cong V_P - n\phi_t \ln\left(\frac{I_P + I_0}{I_0}\right)$$

Diode “ON” voltage drop

Waveforms for $V_P >> n\phi_t$

  

MOSFETs as diodes

  


Channel and extrinsic
diode are in anti-parallel

Channel and extrinsic
diode are in parallel

Weak inversion MOSFET model

$$I_F = 2I_S q'_{IS}$$

 

$$\phi_t = \frac{kT}{q} (= 26 \text{ mV} @ 300\text{K})$$

$$I_S = \mu C'_{ox} n \frac{\phi_t^2}{2} \frac{W}{L} = I_{SQ} \frac{W}{L}$$

$$q'_{IS(D)} = e^{\frac{V_P - V_{S(D)B}}{\phi_t}} \cong e^{\frac{V_{GB} - V_{T0} - nV_{S(D)B}}{n\phi_t}}$$

W, L width, length of the channel

μ mobility, C'_{ox} gate capacitance per unit area, n slope factor ($n = 1.2-1.6$)

V_P pinchoff voltage, V_{T0} threshold voltage

q'_{IS} and q'_{ID} are the normalized carrier densities (to the thermal charge $-nC'_{ox}\phi_t$) at source and drain.

I_S and I_{SQ} are the normalization (specific) and “sheet” normalization currents.

DTMOS diode in WI

- for the DTMOS connection $V_{GB} = V_{DB} = 0$, $v = -V_{SB}$

$$I_{DS} = I_F - I_R = 2I_S e^{-\frac{V_{T0}}{n\phi_t}} \left(e^{\frac{v}{\phi_t}} - 1 \right)$$


- the DTMOS diode behaves as a diode with ideality factor $n = 1$ for low voltage (weak inversion) operation.

$$I_{DS} = I_D = I_0 \left(e^{\frac{v}{\phi_t}} - 1 \right)$$

- Current I_0 of the DTMOS diode can be determined as the saturated drain current of the (conventionally connected) transistor with $V_{GB} = V_{SB} = 0$.

$$I_{DSsat} = I_F = 2I_S e^{-\frac{V_{T0}}{n\phi_t}} = I_0$$

 Standard, low-VT and zero-VT MOSFETs in a 130 nm technology



Rectifier summary

- Analytical model of the rectifier circuit in which the nonlinear device follows the diode Shockley (exponential) equation.
- The model is correct for input voltages down to below the thermal voltage.
- The main design parameter is the diode saturation current I_0 .
- For a DTMOS (WI) diode

$$I_0 \propto \frac{W}{L} e^{\frac{-V_{TO}}{n\phi_t}}$$


we can take advantage of aspect ratio and of different V_T 's



Oscillator outline

- ⇒ Background: minimum supply voltage for FET circuits
- ⇒ MOSFET charge based model
- ⇒ Low voltage operation of the (C)MOS inverter
- ⇒ Ring oscillator
- ⇒ Colpitts oscillator

 Background 1: minimum supply voltage for the CMOS inverter





Prof. James Meindl:
Theoretically, the minimum supply voltage for a CMOS inverter is
 $2 (\ln 2) (kT/q) = 36 \text{ mV}$
at room temperature
(IEEE JSSC, 2000)

CMOS inverter transfer characteristics
(Swanson and Meindl, IEEE JSSC 1972)

Background 2: oscillators with super low supply voltage

Dick Kleijer, available at
  
<http://www.dicks-website.eu/fetosc/enindex.htm>




Oscillator with very high impedance winding ($4\text{ M}\Omega$) transformer running on 5.5 mV supply voltage
Horizontal: 1 ms /div.
Vertical: 200 mV /div.

FET type	Supply voltage	Supply current
2x J 310	19 mV	1.04 mA
3x J 310	17 mV	1.40 mA

MOSFET charge-based model 1

$$I_F = I_S (2q'_{IS} + q'^2_{IS})$$
 
$$I_S = \mu C'_{ox} n \frac{\phi_t^2}{2} \frac{W}{L} = I_{SQ} \frac{W}{L}$$



$$I_R = I_S (2q'_{ID} + q'^2_{ID})$$

$$I_D = I_F - I_R$$

$$I_{F(R)} = I_S (2q'_{IS(D)} + q'^2_{IS(D)})$$


W, L width, length of the channel

μ mobility, C'_{ox} gate capacitance per unit area, n slope factor ($n = 1.2-1.6$)

q'_{IS} and q'_{ID} are the normalized carrier densities (to the thermal charge $-nC'_{ox}\phi_t$) at source and drain.

I_S and I_{SQ} are the normalization (specific) and “sheet” normalization currents.

 MOSFET charge-based model 2 : LF small signal model in the triode region



MOSFET charge-based model 3:the unified charge control model (UCCM)

V_P is the pinch-off voltage

$$\frac{V_P - V_S}{\phi_t} = q'_{IS} - 1 + \ln(q'_{IS})$$

$$\frac{V_P - V_D}{\phi_t} = q'_{ID} - 1 + \ln(q'_{ID})$$

$$g_{ms} = \frac{2I_s}{\phi_t} q'_{IS}$$

$$\frac{V_{DS}}{\phi_t} = q'_{IS} - q'_{ID} + \ln\left(\frac{q'_{IS}}{q'_{ID}}\right)$$


$$g_{md} = \frac{2I_s}{\phi_t} q'_{ID}$$

$$V_{DS} = \frac{\phi_t^2}{2I_s} (g_{ms} - g_{md}) + \phi_t \ln\left(\frac{g_{ms}}{g_{md}}\right)$$

In WI

$$\rightarrow \frac{g_{ms}}{g_{md}} = \frac{q'_{IS}}{q'_{ID}} = e^{\frac{V_{DS}}{\phi_t}}$$

 Low-voltage operation of the MOS inverter (WI / triode region)



$$|A_V| = \frac{g_{mg}}{g_{md}} = \frac{g_{ms} - g_{md}}{n g_{md}} = \frac{1}{n} \left(\frac{g_{ms}}{g_{md}} - 1 \right)$$

weak inversion operation


$$\frac{g_{ms}}{g_{md}} = \frac{q'_{IS}}{q'_{ID}} = e^{\frac{V_{DS}}{\phi_t}}$$

$$|A_V| = \frac{1}{n} \left(e^{\frac{V_{DS}}{\phi_t}} - 1 \right)$$

or

$$V_{DS} = \phi_t \ln(1 + n |A_V|)$$

 Low-voltage operation of the (C)MOS inverter (WI / triode region)




$$V_{DS} = \phi_t \ln(1 + n |A_V|)$$

Minimum supply voltage for amplification $|A_V| = 1$
 ‘ideal’ MOSFET $n = 1$

$$V_{DS} = V_{DD}$$



$$V_{DD\min} = (\ln 2)\phi_t$$

 

$$V_{DS} = V_{DD} / 2$$


$$V_{DD\min} = 2(\ln 2)\phi_t$$

Ring oscillator 1

  


$$\frac{V_{out}}{V_{in}} = -\frac{g_{mg}}{g_{md} + G_p} \frac{1}{1 + j \tan \theta}$$

Minimum gain for oscillation

 

$$\frac{g_{mg}}{g_{md} + G_p} \frac{1}{\sqrt{1 + \tan^2 \theta}} > 1$$

 For the sake of simplicity, we consider $\theta = \pi$.



$$\frac{g_{mg}}{g_{md} + G_p} > 1$$

Ring oscillator 2

Minimum gain for oscillation


$$\frac{g_{mg}}{g_{md} + G_p} = \frac{g_{ms} - g_{md}}{n(g_{md} + G_p)} > 1$$

or

$$\frac{g_{ms}}{g_{md}} \geq 1 + n \left(1 + \frac{G_p}{g_{md}} \right)$$

From the UCCM


$$V_{DD\min} = \frac{\phi_t^2}{2I_S} n(g_{md} + G_p) + \phi_t \ln \left[1 + n \left(1 + \frac{G_p}{g_{md}} \right) \right]$$

 
SI **WI**

Considering high Q inductor ($G_p \ll g_{md}$) and WI operation and $n = 1$

$$V_{DD\min} = (\ln 2) \phi_t$$

Colpitts oscillator 1

 


**For high Q inductor ($G_{inductor} \ll g_{md}$)
and WI operation**

$$V_{DD\min} \cong \phi_t \ln \left(1 + n \frac{C_2}{C_1} \right)$$

Colpitts oscillator 2

TRANSISTOR CHARACTERISTICS MEASURED FOR $V_{DD} = 20 \text{ mV}$ AT
 $T = 23^\circ\text{C}$.

Parameter	Value
I_S (Specific Current)	$11.18 \mu\text{A}$
V_{TH} (Threshold Voltage)	59 mV
g_{ms} (Source Transconductance)	$520 \mu\text{A/V}$
g_{md} (Drain Transconductance)	$325 \mu\text{A/V}$
n (Slope factor)	1.6

 

Photograph of the oscillator working from a thermoelectric generator at $T=24^\circ\text{C}$.

Oscillator summary

- There is no hard low voltage limit for analog MOS circuits (oscillators can operate with supply voltage under kT/q)
- The ideal active device for low voltage operation is a MOSFET with threshold voltage near zero (for WI operation at low supply voltage)
- The charge based MOSFET model is very convenient for the design of ultra-low-voltage circuits (operation in triode region/ WI)

References

- M. C. Schneider and C. Galup-Montoro, *CMOS Analog Design Using All-Region MOSFET Modeling*, Cambridge University Press, 2010.
- A. J. Cardoso, L. G. de Carli, C. Galup-Montoro, and M. C. Schneider, "Analysis of the rectifier circuit valid down to its low-voltage limit," *IEEE Transactions on Circuits and Systems I*, 2011.
- F. R. de Sousa, M. B. Machado, C. Galup-Montoro, "A 20 mV Colpitts Oscillator powered by a thermoelectric generator, submitted to *ISCAS 2012*.